

# UNIVERSITY OF MIAMI

Department of Electrical and Computer Engineering  
EEN 311

You will get the full points for this experiment if you complete the Preliminary Work.

Name: \_\_\_\_\_  
Section: \_\_\_\_\_  
Date: \_\_\_\_\_

## EXPERIMENT 6

NPN PN2222  
 $V_{be}=V_{drop}=0.7V$

### DC AND AC CHARACTERISTICS OF TRANSISTORS

**PURPOSE:** In the first part of this experiment, the common-emitter output characteristics of an npn bipolar junction transistor will be investigated using a transistor curve tracer. The purpose of the second part is to verify the voltage and currents in a fixed bias circuit. In spite of its simplicity, a fixed bias circuit does not effectively stabilize a transistor's quiescent point. Consequently, the Q-point is affected by the transistor's current gain  $\beta$ . In the final part, the voltages and currents in a self bias circuit will be verified. This bias scheme is often used because the base current is made small compared to the currents through the two base "voltage-divider" resistors. Consequently, the base voltage, and therefore the collector current, is stabilized against changes in the transistor beta.


#### Preliminary Work

- 1) Using the formulas

$$I_E = I_C + I_B, \quad \alpha = \frac{I_C}{I_E}, \quad \beta = h_{FE} = \frac{I_C}{I_B},$$

Where  $I_C$ ,  $I_E$ , and  $I_B$  are the collector, emitter, and base currents of a BJT, respectively, find:


- $\alpha$  in terms of  $\beta$ .
  - $\beta$  in terms of  $\alpha$ .
- 2) Find the expressions for  $R_B$  and  $R_C$  in terms of  $\beta$ ,  $V_{CC}$ ,  $V_{CEQ}$ , and  $I_{CQ}$  for the fixed bias circuit of Fig. 3.1. Assume that  $V_{BE} = 0.7V$ ;  $V_{CEQ}$  and  $I_{CQ}$  are the desired quiescent point values.

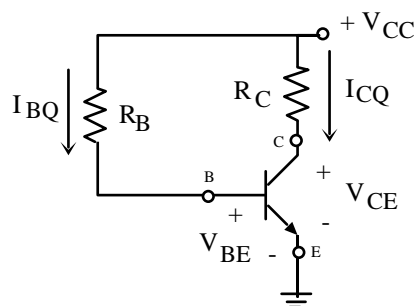

**Figure 3.1** Simple Fixed Bias Circuit.

3) The following figure is a self biased common-emitter amplifier stage.

- a) Find the Thevenin Equivalent of the part of the circuit between points a & b as shown.

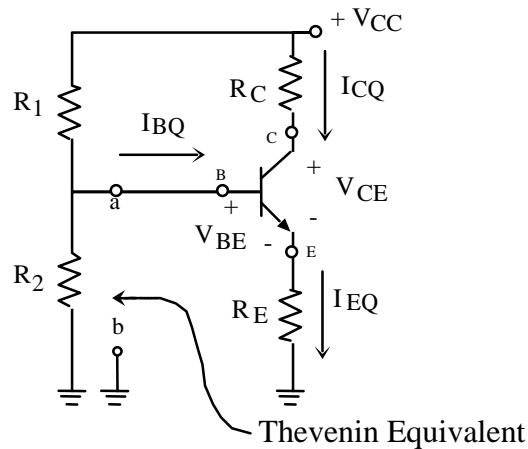

**Figure 3.2** Self Biased Common-Emitter Amplifier


- b) Find the expressions for  $R_C$  and  $R_E$  in terms of  $V_{CEQ}$ ,  $I_{CQ}$  (the desired Q-point values), and  $V_{CC}$ . Assume that  $\beta \gg 1$ ,  $I_{CQ} \cong I_{EQ}$ , and  $V_{EQ} = 0.1V_{CC}$ .
- c) Redraw the circuit replacing the part to the left of points a & b by the Thevenin Equivalent  $V_{Th}$  and  $R_{Th}$ . Find the expression for  $V_{Th}$  in terms of  $V_{BE}$ ,  $I_{CQ}$ ,  $\beta$ , and  $R_E$ . The base-to-emitter voltage drop,  $V_{BE}$ , is given by  $V_{BE} \cong 0.7$  V for a Si transistor, when operating properly. Also, choose  $R_{Th}$  as  $R_{Th} = 0.1(\beta + 1)R_E$ . This selection for  $R_{Th}$  will provide good voltage stability with respect to temperature. Q-point stability and temperature effects will be investigated in Experiment 13.
- d) Justify the selection  $R_{Th} = 0.1(\beta + 1)R_E$  mentioned in part (c).
- e) Find the expressions for  $R_1$  and  $R_2$  in terms of  $R_{Th}$ ,  $V_{Th}$ , and  $V_{CC}$  by solving the expressions for  $R_{Th}$  and  $V_{Th}$  found in part (a) simultaneously.

## Experimental Procedure

### I. BJT Characteristics:


The output characteristics ( $I_C$  vs  $V_{CE}$  for different  $I_B$ 's) of the given transistor will be investigated using a *Transistor Curve Tracer*.

- a) Connect your transistor to the transistor test panel.

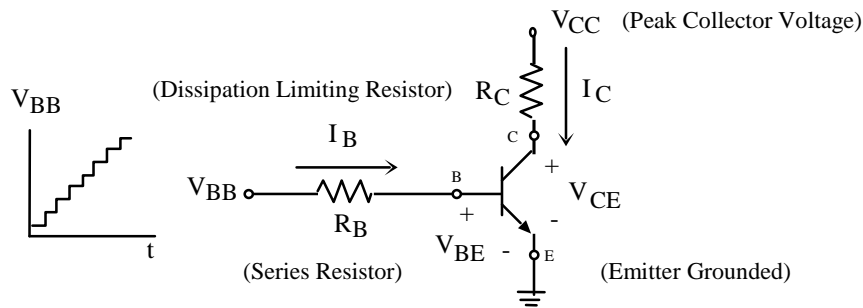

**Figure 3.3** Configuration for Transistor Connection.

- b) Obtain a copy of the characteristics displayed on the curve tracer. Collect your data in Table 3.1 (this will help you determine  $\beta_{DC}$  and  $\beta_{AC}$ , the static forward current ratio and the small-signal short circuited forward current ratio, respectively). Take readings for at least three different base current values from the output characteristics at  $V_{CEQ}$ . Remember that the readings should be made for a constant  $V_{CE}$  voltage and around the  $I_{CQ}$  of interest (see Fig. 3.4).  $h_{fe}$  will be calculated for two Q-points:  $V_{CEQ} = 10$  V,  $I_{CQ} = 1$  mA; and  $V_{CEQ} = 10$  V,  $I_{CQ} = 10$  mA.

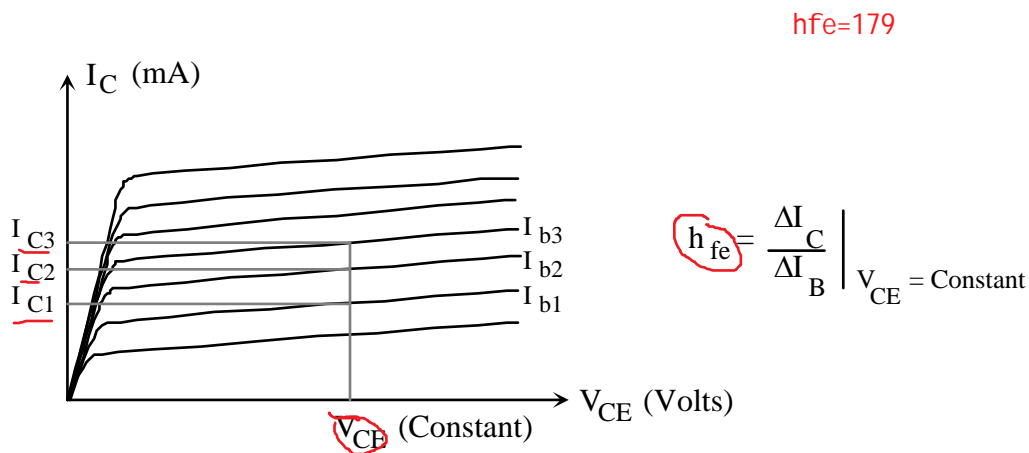

**Figure 3.4** Typical BJT  $V_{CE}$  vs  $I_C$  characteristics.

$V_{CEQ} = 10V, I_{CQ} = 1mA$		$V_{CEQ} = 10V, I_{CQ} = 10mA$	
$I_B (\mu A)$	$I_C (mA)$	$I_B (\mu A)$	$I_C (mA)$
		55 $\mu A$	9.8 mA
	1.0	56.1 $\mu A$	10.6

**Table 3.1** Data for Calculating  $\beta_{DC}$  and  $\beta_{AC}$ .

- c) Using the data in the table above, calculate three different values for  $\beta_{AC}$  as  $\beta_{AC} = h_{fe} = \Delta I_C / \Delta I_B$ . Then find the average of the three and record your experimental value for it below

At  $I_{CQ} = 1 \text{ mA}$  and  $V_{CEQ} = 10 \text{ V}$ :  $\beta_{AC} = \underline{179}$

At  $I_{CQ} = 10 \text{ mA}$  and  $V_{CEQ} = 10 \text{ V}$ :  $\beta_{AC} = \underline{\hspace{2cm}}$

- d) Using the data in Table 3.1, calculate  $\beta_{DC}$  as  $\beta_{DC} = I_{CQ} / I_{BQ}$  for  $I_{CQ} = 1 \text{ mA}$  and  $V_{CEQ} = 10 \text{ V}$ .

At  $I_{CQ} = 1 \text{ mA}$  and  $V_{CEQ} = 10 \text{ V}$ :  $\beta_{DC} = \underline{\hspace{2cm}}$

- e) Repeat part (d) for  $I_{CQ} = 10 \text{ mA}$  and  $V_{CEQ} = 10 \text{ V}$ .

At  $I_{CQ} = 10 \text{ mA}$  and  $V_{CEQ} = 10 \text{ V}$ :  $\beta_{DC} = \underline{\hspace{2cm}}$

## II. Fixed Bias Circuit:

- a) Using the results of the second part of your Preliminary Work, select  $R_B$  and  $R_C$  for the following fixed bias circuit, given that

$$V_{CC} = 20 \text{ V}, \quad V_{CEQ} = 10 \text{ V}, \quad I_{CQ} = 10 \text{ mA}, \quad V_{BE} = 0.7 \text{ V}.$$

For  $\beta$ , use the result of Experimental Procedure part I.e.

LM741  
LM324

$$\beta = 179$$


$$R_B = (V_{CC} - V_{BE}) / I_B$$

$$R_C = (V_{CC} - V_{CE}) / I_C$$

$$I_C = \beta I_B$$

$$R_B = 179 * (20 - 0.7) / (10 * 10^{-3}) = 345.47K$$

$$R_C = 1K$$

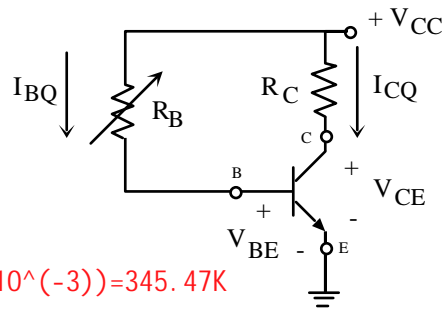

$$I_{CQ} = 10mA$$

$$R_C = \underline{\hspace{2cm}} \quad R_B = \underline{\hspace{2cm}}$$

**Figure 3.5** Fixed Bias Circuit.

**IMPORTANT:** Setup the circuit in Fig 3.5 and verify that the operating point  $V_{CEQ}$  and  $I_{CQ}$  are reasonably close to the desired design values used in (a), proceed with the measurements. If not, vary  $R_B$  until the desired values are obtained. Make a note of this fact and record the initial and final values of  $R_B$ .

$$R_{Bi} = \underline{\hspace{2cm}}$$

$$R_{Bf} = \underline{\hspace{2cm}}$$

b) Measure and calculate the following:

$$V_{CEQ} = \underline{\hspace{2cm}}$$

$$V_{RC} = \underline{\hspace{2cm}}$$

$$V_{RB} = \underline{\hspace{2cm}}$$

$$V_{BE} = \underline{\hspace{2cm}}$$

$$I_{CQ} = \frac{V_{RC}}{R_C} = \underline{10mA}$$

$$I_{BQ} = \frac{V_{RB}}{R_B} = \underline{56.1\mu A}$$


$$I_{BQ} = \frac{V_{RB}}{R_B} = \underline{52.9\mu A}$$

### III. Self Bias Circuit:

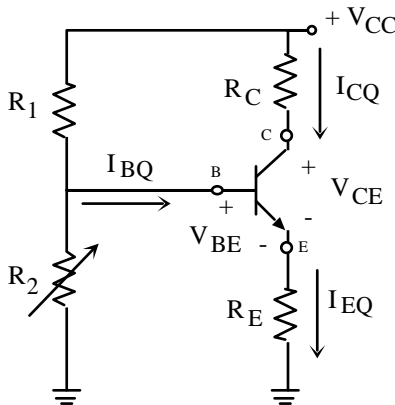- 1) Using the results of the third part of your Preliminary Work, select  $R_C$ ,  $R_E$ ,  $R_1$ , and  $R_2$  for the following self bias circuit, given that

$$V_{CC} = 20 \text{ V}, \quad V_{CEQ} = 10 \text{ V}, \quad I_{CQ} = 1 \text{ mA}, \quad V_{BE} = 0.7 \text{ V}.$$

For  $\beta$ , use the result of Experimental Procedure part I.d.



$$\begin{aligned} V_{CC} &= 20\text{V} \\ V_{CEQ} &= 10\text{V} \\ I_{CQ} &= 1\text{mA} \\ V_{BE} &= 0.7\text{V} \\ \beta &= 179 \end{aligned}$$

$$\begin{aligned} R_{Th} &= 0.1 * (\beta + 1) * R_E \\ R_{Th} &= (R_1 * R_2) / (R_1 + R_2) \\ V_{Th} &= V_{CC} * R_2 / (R_1 + R_2) \\ R_1 &= V_{CC} * R_{Th} / V_{Th} = 249.7\text{K} \\ R_2 &= V_{CC} * R_{Th} / (V_{CC} - V_{Th}) = 42.056\text{K} \\ R_C &= (0.9V_{CC} - V_{CEQ}) / I_{CQ} = 8\text{K} \\ R_E &= (0.1V_{CC}) / I_{CQ} = 1.994\text{K} \end{aligned}$$

$$R_C = \underline{\hspace{2cm}} \quad R_E = \underline{\hspace{2cm}} \quad R_1 = \underline{\hspace{2cm}} \quad R_2 = \underline{\hspace{2cm}}$$

**Figure 3.6** Self Bias Circuit.

**IMPORTANT:** Setup the circuit in Fig 3.6 and verify that the operating point values  $V_{CEQ}$  and  $I_{CQ}$  are reasonably close to the desired design values, proceed with the measurements. If not, vary  $R_2$  until the desired values are obtained. Make a note of this fact and record the initial and final values of  $R_2$ .

$$R_{2i} = \underline{\hspace{2cm}} \quad R_{2f} = \underline{\hspace{2cm}}$$

- 2) Measure and calculate the following:

$$V_{CEQ} = \underline{\hspace{2cm}}$$

$$V_{RC} = \underline{\hspace{2cm}}$$

$$V_{RE} = \underline{\hspace{2cm}}$$

$$V_{BE} = \underline{\hspace{2cm}}$$

$$I_{CQ} = \frac{V_{RC}}{R_C} = \underline{\hspace{2cm}}$$

$$I_{EQ} = \frac{V_{RE}}{R_E} = \underline{\hspace{2cm}}$$

### ***Discussion of the Results***

- 1) If you had to vary  $R_B$  and/or  $R_2$  in Experimental Procedure parts II.b and III.b in order to obtain the desired values of  $V_{CEQ}$  and  $I_{CQ}$ , give possible reasons why your original design did not work and explain how changing  $R_B$  and/or  $R_2$  helped to obtain the desired values.
- 2) Using the results of Experimental Procedure part II.b, calculate the static forward current gain of the transistor as  $\beta = \frac{I_{CQ}}{I_{BQ}}$ . Compare this to the one found in Experimental Procedure part I.c when  $V_{CEQ} = 10\text{ V}$  and  $I_{CQ} = 10\text{ mA}$  by finding the percentage error. What is the difference between the equation above and the one given by

$$\beta_{AC} = \frac{\Delta I_C}{\Delta I_B} ?$$

- 3) a) What is the range of the output active region for the fixed bias circuit if the output voltage is taken between the collector and the common ground, instead of between the collector and the emitter (i.e.,  $V_C$ , instead of  $V_{CE}$ )?  
Assume that at saturation,  $V_{CE} = 0\text{ V}$ .  
b) Repeat (a) for the self bias circuit.
- 4) Write a conclusion.